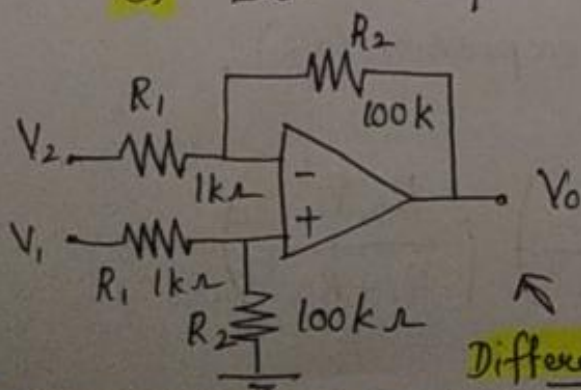


Instrumentation Amplifier

- * For industrial and consumer applications, it is necessary to measure and control physical quantities like temperature, humidity, light intensity, water flow etc.
- * These physical quantities are usually measured with the help of transducers.
- * The output of the transducer has to be amplified, so that it can drive the display system. This function is performed by an instrumentation amplifier.

Features of an instrumentation amplifier

- (1) High gain accuracy.
- (2) High CMRR.
- (3) High gain stability with low temperature co-efficient
- (4) Low dc offset
- (5) Low output impedance.



$V_1 \rightarrow \text{i/p impedance} \rightarrow (100+1) = 101k\Omega$


$V_2 \rightarrow \text{i/p impedance} \rightarrow 1k\Omega = 1k\Omega$

\Downarrow creates

Loading effect

Differential Amplifier

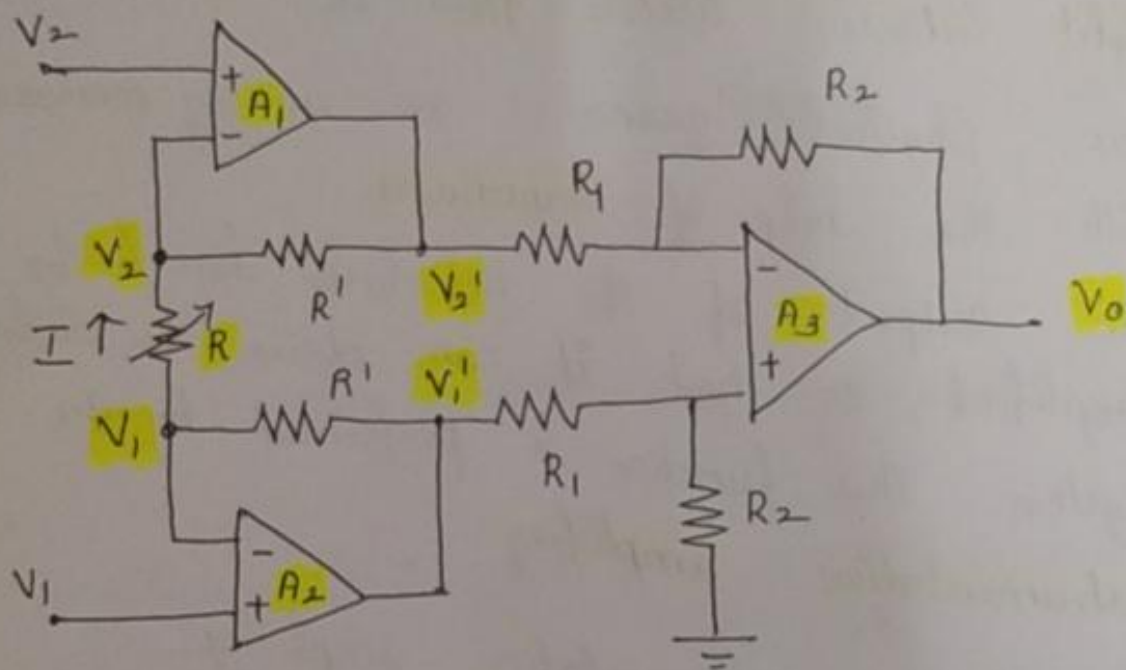* To avoid this loading effect, high resistance buffer is used preceding to the differential amplifier, that circuit is called instrumentation amplifier.



* For $V_1 = V_2$, under common-mode condition, no current flows through R & R' , so A_1 & A_2 act as voltage follower.

* If $V_1 \neq V_2$, current flows in R & R' , &
 $(V_2' - V_1') > (V_2 - V_1)$.

Let us,

Write the output voltage expression (V_0),

$$V_0 = - \left(\frac{R_2}{R_1} \right) \underset{\substack{\text{inv. gain} \\ \downarrow \text{ i/p}}}{V_2'} + \left(1 + \frac{R_2}{R_1} \right) \left(\underset{\substack{\text{non-inv. gain} \\ \downarrow \text{ i/p}}}{\frac{R_2 V_1'}{R_1 + R_2}} \right)$$

$$\begin{aligned}\therefore V_o &= -\frac{R_2}{R_1} V_2' + \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_2 V_1'}{R_1 + R_2} \right) \\ &= -\frac{R_2}{R_1} V_2' + \frac{R_2}{R_1} V_1'\end{aligned}$$

$$V_o = \frac{R_2}{R_1} (V_1' - V_2') \rightarrow (1)$$

* The current flows through 'R' expressed as

$$I = \frac{(V_1 - V_2)}{R}$$

$$\therefore V_1' = R'I + V_1 = \frac{R'}{R} (V_1 - V_2) + V_1 \rightarrow (2)$$

$$V_2' = -R'I + V_2 = -\frac{R'}{R} (V_1 - V_2) + V_2 \rightarrow (3)$$

Substitute equation (2) and (3) in (1), we get

$$\begin{aligned}V_o &= \frac{R_2}{R_1} (V_1' - V_2') \\ &= \frac{R_2}{R_1} \left[\left(\frac{R'}{R} (V_1 - V_2) + V_1 \right) - \left(-\frac{R'}{R} (V_1 - V_2) + V_2 \right) \right] \\ &= \frac{R_2}{R_1} \left[\frac{2R'}{R} (V_1 - V_2) + (V_1 - V_2) \right]\end{aligned}$$

$$V_o = \frac{R_2}{R_1} (V_1 - V_2) \left[1 + \frac{2R'}{R} \right] \rightarrow (4)$$

In equation (4), if we choose

$$R_1 = R_2 = 25k\Omega$$

$$R' = 25k\Omega$$


$$R = 50\Omega, \text{ then}$$

$$\begin{aligned} \text{Gain} = \frac{V_o}{V_i} &= \frac{R_2}{R_1} \left(1 + \frac{2R'}{R} \right) = \frac{25k}{25k} \left(1 + \frac{2(25k)}{50} \right) \\ &= \left(1 + \frac{50k}{50\Omega} \right) \end{aligned}$$

$$\boxed{\text{Gain} = 1001}$$

* The differential gain of this instrumentation amplifier is varied by replacing the resistance 'R' by a potentiometer.

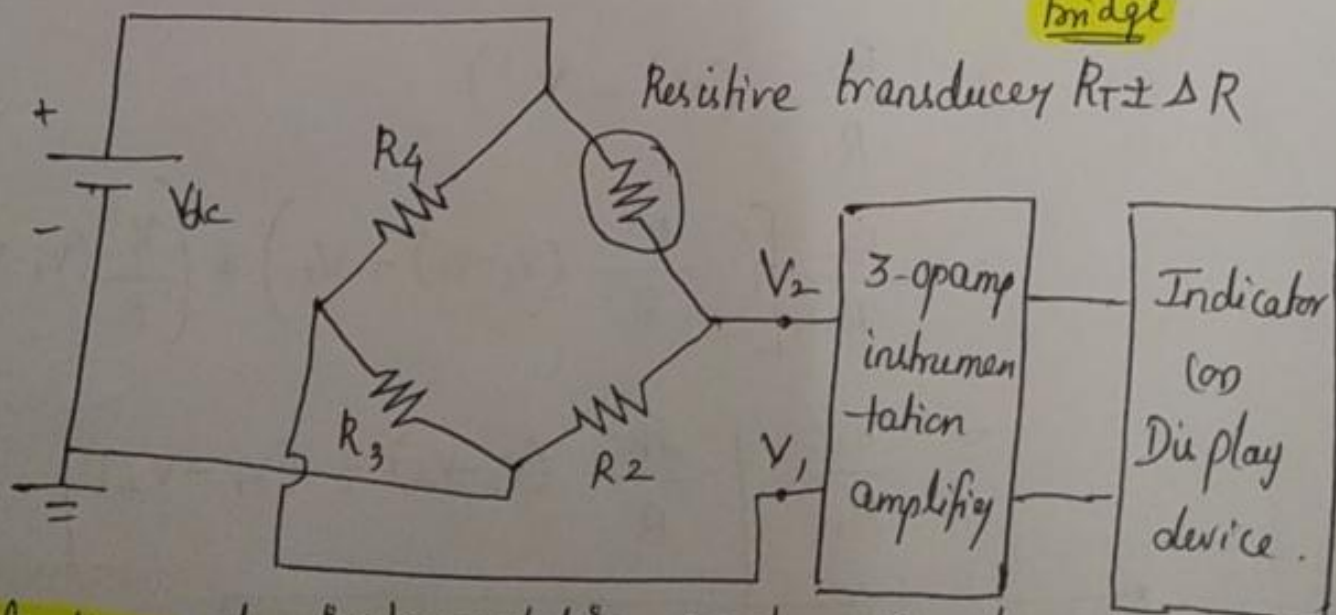
Instrumentation amplifier using transducer bridge



Applications of instrumentation ampl. with transducer bridge:

Temperature indicator, Temperature controller, Light intensity meter, Analog weighing scale, Measurement of flow of electricity & thermal conductivity

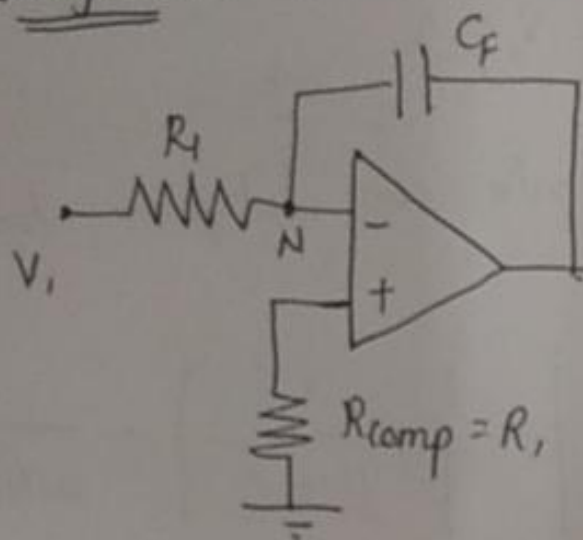Integrator.. (Low pass filter) \rightarrow It provides an o/p voltage which is proportional to the time integral of the i/p and $R_1 C_f$ is the time constant of the integrator.



* The Nodal equation at node N, is

$$\frac{V_i}{R_1} + C_f \frac{dv_o}{dt} = 0$$

$$\frac{dv_o}{dt} = -\frac{1}{R_1 C_f} V_i$$

Integrating both sides, we get

$$\int_0^t \frac{dv_o}{dt} dt = -\frac{1}{R_1 C_f} \int_0^t V_i dt$$

$$V_o(t) = -\frac{1}{R_1 C_f} \int_0^t V_i dt + \underbrace{V_o(0)}_{\text{initial o/p voltage}}$$

In frequency domain,

$$V_o(s) = -\frac{1}{s R_1 C_f} V_i(s)$$


In steady state, put $s = j\omega$,

$$V_o(j\omega) = - \frac{1}{j\omega R_i C_f} V_i(j\omega)$$

The magnitude of the gain (or Integrator transfer function) is,

$$|A| = \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = \left| - \frac{1}{j\omega R_i C_f} \right| = \frac{1}{\omega R_i C_f}$$

Differentiator: (High pass filter)

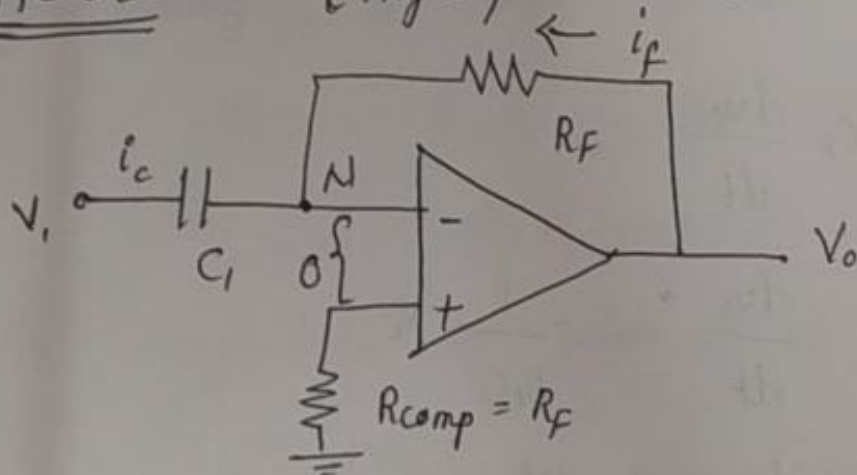

The o/p voltage v_o is a constant $(-R_F C_i)$ times the derivative of the input voltage v_i . The circuit is a differentiator.

Analysis:

The node N is at virtual ground $v_N = 0$. The current i_c through the capacitor is,

$$i_c = C_i \frac{d}{dt} (v_i - v_N) = C_i \frac{dv_i}{dt}$$

The nodal equation at node N,

$$C_1 \frac{dv_i}{dt} + \frac{V_o}{R_F} = 0.$$

$$\therefore V_o = -R_F C_1 \frac{dv_i}{dt}$$

In frequency domain,

$$V_o(s) = -R_F C_1 s V_i(s)$$

In steady state, put $s = j\omega$, then

$$V_o(s) = -R_F C_1 s V_i(s) \text{ becomes}$$

$$V_o(j\omega) = -R_F C_1 (j\omega) V_i(j\omega).$$

The magnitude of gain A of the differentiator is

$$|A| = \left| \frac{V_o}{V_i} \right| = -j\omega R_F C_1 = \omega R_F C_1.$$

In the frequency response of the Op-amp, the frequency can be written as

$$f_a = \frac{1}{2\pi R_F C_1}$$

Inverting Summing Amplifier

A typical summing amplifier with three input voltages V_1 , V_2 and V_3 , three input resistors R_1 , R_2 , R_3 and a feedback resistor R_f is shown in Fig. 4.2 (a). The following analysis is carried out assuming that the op-amp is an ideal one, that is, $A_{OL} = \infty$ and $R_i = \infty$. Since the input bias current is assumed to be zero, there is no voltage drop across the resistor R_{comp} and hence the non-inverting input terminal is at ground potential.

The voltage at node 'a' is zero as the non-inverting input terminal is grounded. The nodal equation by KCL at node 'a' is

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_o}{R_f} = 0$$

$$\text{or,} \quad V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right) \quad (4.1)$$

Thus the output is an inverted, weighted sum of the inputs. In the special case, when $R_1 = R_2 = R_3 = R_f$, we have

$$V_o = - (V_1 + V_2 + V_3) \quad (4.2)$$

in which case the output V_o is the inverted sum of the input signals. We may also set

$$R_1 = R_2 = R_3 = 3R_f$$

in which case

$$V_o = - \left(\frac{V_1 + V_2 + V_3}{3} \right) \quad (4.3)$$

Thus the output is the average of the input signals (inverted). In a practical circuit, input bias current compensating resistor R_{comp} should be provided as discussed in Sec. 3.2.1. To find R_{comp} , make all inputs $V_1 = V_2 = V_3 = 0$. So the effective input resistance $R_i = R_1 \parallel R_2 \parallel R_3$. Therefore, $R_{comp} = R_i \parallel R_f = R_1 \parallel R_2 \parallel R_3 \parallel R_f$.

Example 4.1

Design an adder circuit using an op-amp to get the output expression as

$$V_o = - (0.1 V_1 + V_2 + 10 V_3)$$

where V_1 , V_2 , and V_3 are the inputs.

Solution

The output in Fig. 4.2 (a) is

$$V_o = - [(R_f/R_1) V_1 + (R_f/R_2) V_2 + (R_f/R_3) V_3]$$

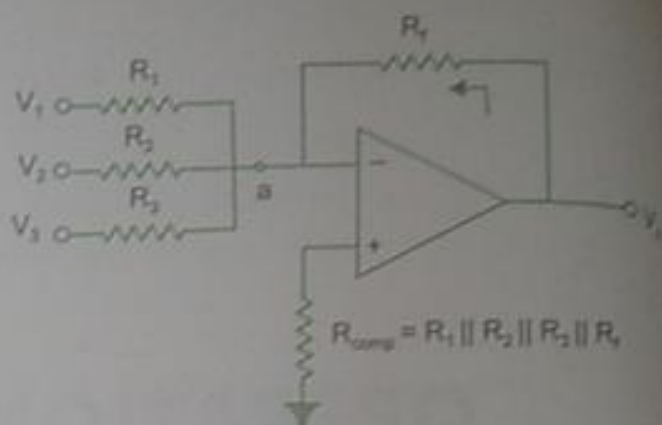


Fig. 4.2 (a) Inverting summing amplifier

say

$$R_f = 10 \text{ k}\Omega, R_1 = 100 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega, R_3 = 1 \text{ k}\Omega$$

Then the desired output expression is obtained.

Non-inverting Summing Amplifier

A summer that gives a non-inverted sum is the non-inverting summing amplifier of Fig. 4.2 (b). Let the voltage at the $(-)$ input terminal be V_a . The voltage at $(+)$ input terminal will also be V_a . The nodal equation at node 'a' is given by

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3} = 0$$

from which we have,

$$V_a = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

The op-amp and two resistors R_f and R constitute a non-inverting amplifier with

$$V_o = \left(1 + \frac{R_f}{R}\right) V_a$$

Therefore, the output voltage is,

$$V_o = \left(1 + \frac{R_f}{R}\right) \frac{\left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}\right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

which is a non-inverted weighted sum of inputs.

Let $R_1 = R_2 = R_3 = R = R_f/2$, then $V_o = V_1 + V_2 + V_3$

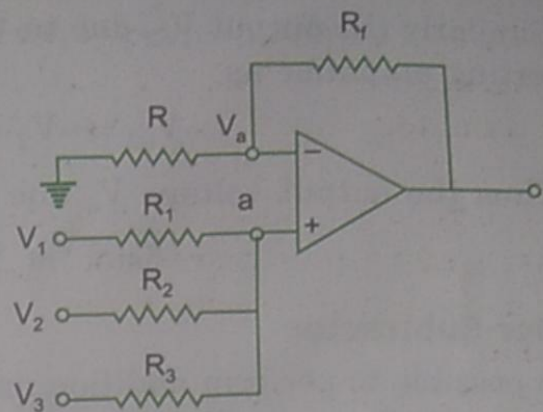


Fig. 4.2 (b) Non-inverting summing amplifier